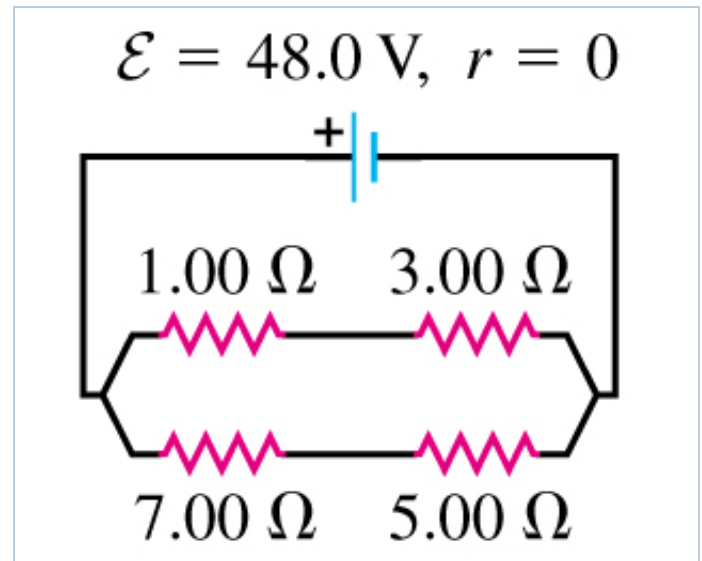


HW due 6/20**Due: 7:00am on Monday, June 20, 2016**To understand how points are awarded, read the [Grading Policy](#) for this assignment.**Exercise 26.14****Part A**

Compute the equivalent resistance of the network in the figure.
The battery has negligible internal resistance.



ANSWER:

$$R_{\text{eq}} = 3.00 \, \Omega$$

Correct**Part B**

Find the current in $1.00 \, \Omega$ resistor.

ANSWER:

$$I = 12.0 \, \text{A}$$

Correct**Part C**

Find the current in $3.00 \, \Omega$ resistor.

ANSWER:

$$I = 12.0 \text{ A}$$

Correct

Part DFind the current in 5.00Ω resistor.

ANSWER:

$$I = 4.00 \text{ A}$$

Correct

Part EFind the current in 7.00Ω resistor.

ANSWER:

$$I = 4.00 \text{ A}$$

Correct

Problem 25.64

A person with body resistance between his hands of $10 \text{ k}\Omega$ accidentally grasps the terminals of a 16-kV power supply.

Part A

If the internal resistance of the power supply is 2500Ω , what is the current through the person's body?

Express your answer using two significant figures.

ANSWER:

$$I = 1.3 \text{ A}$$

Correct

Part B

What is the power dissipated in his body?

Express your answer using two significant figures.

ANSWER:

$$P = 1.6 \times 10^4 \text{ W}$$

Correct

Part C

If the power supply is to be made safe by increasing its internal resistance, what should the internal resistance be for the maximum current in the above situation to be $I_{\text{max}} = 1.00 \text{ mA}$ or less?

Express your answer using two significant figures.

ANSWER:


$$r = 1.6 \times 10^7 \Omega$$

Correct

Exercise 26.28

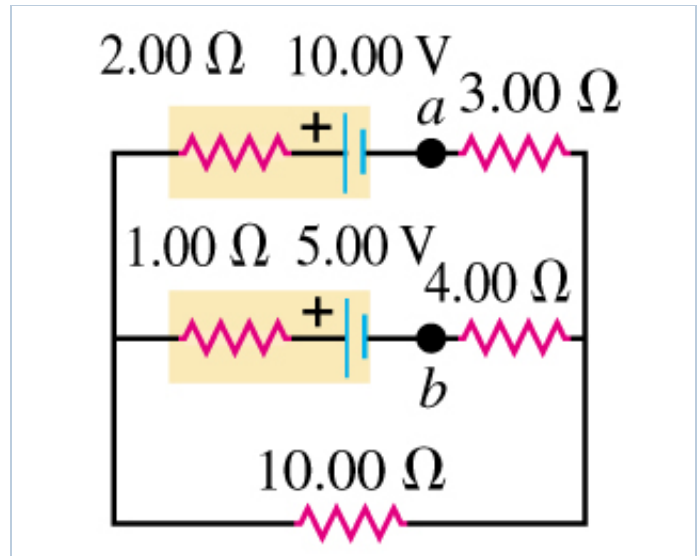Part A

In the circuit shown in the figure , find the magnitude of current in the upper branch.



ANSWER:

$$I = 0.800 \text{ A}$$

Correct**Part B**

Find the magnitude of current in the middle branch.

ANSWER:

$$I = 0.200 \text{ A}$$

Correct**Part C**

Find the magnitude of current in the lower branch.

ANSWER:

$$I = 0.600 \text{ A}$$

Correct**Part D**

What is the potential difference V_{ab} of point a relative to point b ?

ANSWER:

$$V_{ab} = -3.20 \text{ V}$$

Correct

Score Summary:

Your score on this assignment is 100%.

You received 15 out of a possible total of 15 points.