

## Select the one response that best answers each question.

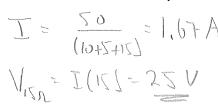1) For the circuit shown in the figure, the capacitors are all initially uncharged, the connecting leads have no resistance, the battery has no appreciable internal resistance, and the switch *S* is originally open.




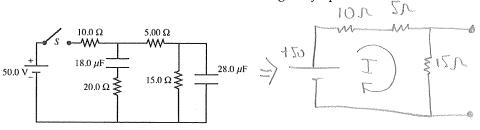

After the switch S has been closed for a very long time, what is the voltage across the  $28.0-\mu F$  capacitor?  $\Delta M \in \Delta S$ 

- A) 37.5 V
- B) 25.0 V
- C) 0.00 V
- D) 3.33 V
- E) 50.0 V

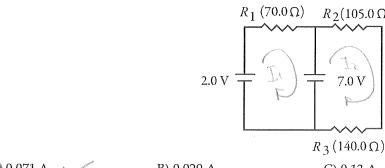2) For the circuit shown in the figure, what is the current through resistor  $R_1$ ?




luce # 12-70I1-7:0

11 J. J. C. O. O. A. A. Picked wrong direction &

- (A) 0.071 A
- B) 0.029 A
- C) 0.13 A

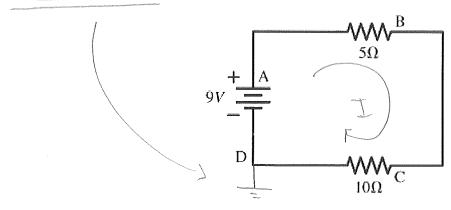- D) 0.016 A
- 3) A 9 Volt battery is hooked up to two resistors in series. One has a resistance of 5 ohms, and the other has a resistance of 10 ohms. Several locations along the circuit are marked with letters, as shown below. If the voltage is zero at the negative terminal of the battery, the voltage at location B is \_\_\_\_\_\_\_.





T= 9 = 0,6A Vg: +9-5(6)=+6Y

- A) zero.
- C) 4.5 Volts.

- B) greater than 4.5 Volts.
- D) less than 4.5 Volts.

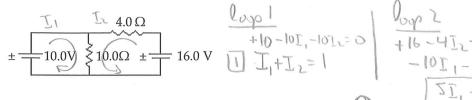4) In the figure below, what is the current through the 4.0  $\Omega$  resistor?



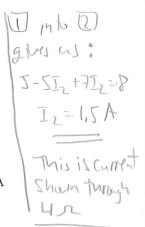


A) 0.43 A

B) 1.1 A

(C) 1.5 A

5) If the voltage at a point in space is zero, then the electric field must be \_\_\_\_\_

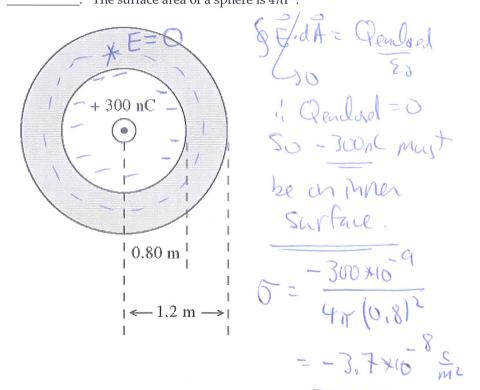- A) negative.
- B) positive.
- C) uniform.
- D) zero.
- (E) it is impossible to determine based on the information given.
- 6) A hollow conducting spherical shell has radii of 0.80 m and 1.20 m, as shown in the figure. The sphere carries an excess charge of –500 nC. A point charge of +300 nC is present at the center. The surface charge density on the inner spherical surface is closest to \_\_\_\_\_\_. The surface area of a sphere is  $4\pi r^2$ .



A) zero.


B)  $+4.0 \times 10^{-8}$  C/m<sup>2</sup>.

(C) -4.0 × 10<sup>-8</sup> C/ m<sup>2</sup>.

D)  $+6.0 \times 10^{-8}$  C/ m<sup>2</sup>.

E)  $-6.0 \times 10^{-8}$  C/ m<sup>2</sup>.

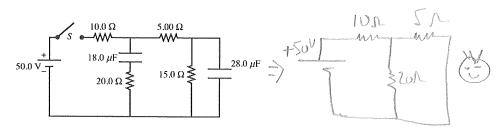
7) For the circuit shown in the figure, the capacitors are all initially uncharged, the connecting leads have no resistance, the battery has no appreciable internal resistance, and the switch S is originally open.



Just after closing the switch *S*, what is the current in the 15.0- $\Omega$  resistor?

- A) 1.67 A
- B) 0.00 A (5 hoted 1
- D) 5.00 A
- E) 2.50 A

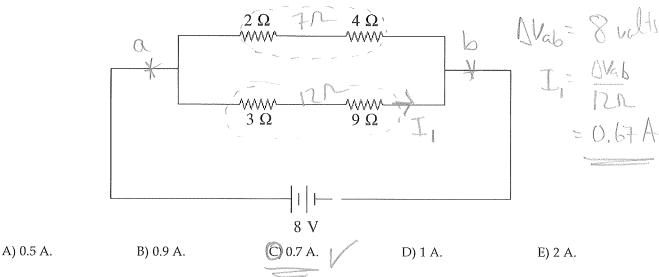8) Four resistors are connected across an 8V battery as shown in the figure. The current through the 9- $\Omega$  resistor is closest to



9) A device with a resistance of 200.0  $k\Omega$  is connected to a 9.0 V battery. How much power does the device use?

- A) 1800 kW
- (B) 0.41 mW (C) 0.045 mW (4.05 × 10 7 web)

10) In a certain region, the electric potential due to a charge distribution is given by the equation  $V(x,y,z) = 3x^2y^2 + 10$ e y-component of the electric tiesu ...  $E_{y} = -\frac{\partial V}{\partial y} = -6\chi^{2}y - \chi^{2}$   $Q(4,3,2) + h_{12} + h_{13} + h_{14} + h_{15} = -h_{14} + h_{15} + h_{15$  $yz^3$  -  $2z^3x$ . The units are SI. What is the y-component of the electric field at the point x=4, y=3, z=2?

- A) 296 V/m
- B) 392 V/m
- C) -392 V/m



- D) No way to tell with out defining the zero voltage point.
- (E) -296 V/m

- 11) If the potential in a region is given by  $V(x,y,z) = xy 3yz^{-2} + 4$ , then the y component of the electric field in that Again E  $3x^{-2} - x$   $D = xy + 3yz^{-2}$ region is \_
  - A)  $x 3z^{-2}$
  - C)  $-xy^2/2 + 3y^2/z^2 4y$

"MOVES" is a better Word 12) A negative charge is moved from point A to point B along a path where the voltage is constant. Which of the following statements must be true for this case?

 $\langle$  A) Work is required to move the negative charge from point A to point B.

B) The negative charge performs work in moving from point *A* to point *B*.

(C) No work is required to move the negative charge from point A to point B.

 $\times$  D) The work done on the charge depends on the distance between A and B.

 $\langle$  E) Work is done in moving the negative charge from point A to point B.

13) The capacitors in the network shown in the figure all have a capacitance of 5.0  $\mu$ F. What is the equivalent capacitance, C<sub>ab</sub>, of this capacitor network?


1'C = 3uF

B) 10 μF C) 1.0 µF D) 3.0 µF

A) 20 μF

E)  $5.0 \, \mu F$ 

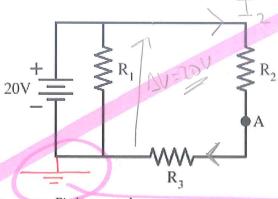14) In the circuit below, the resistor R<sub>2</sub> is adjustable. As its resistance is made larger, the voltage at point A





(A) decreases.

B) does not change.

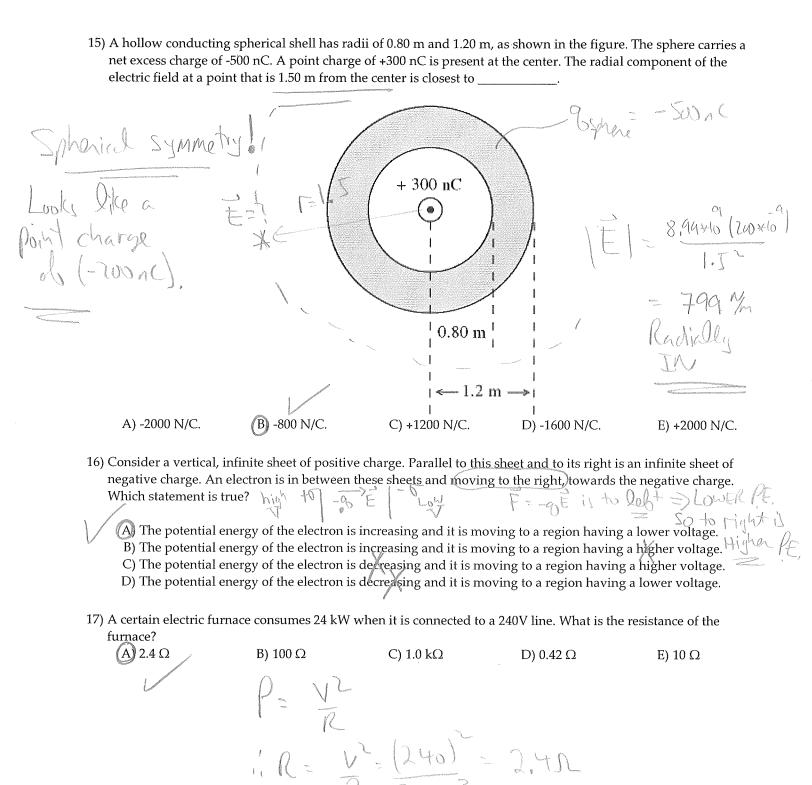C) increases.


ground we can answer the If R gets larger, Iz gets al. This will get smaller.




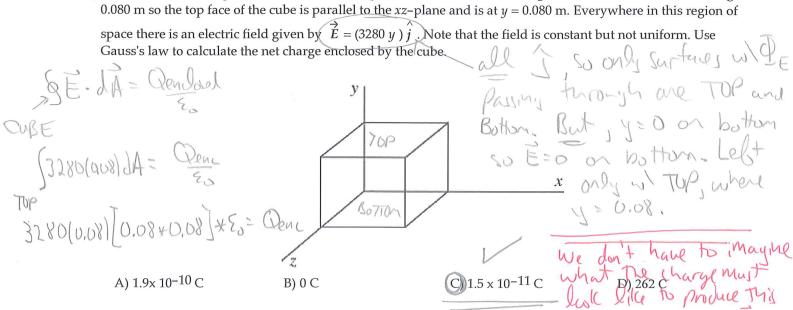

18) The cube of insulating material shown in the figure has one corner at the origin. Each side of the cube has length

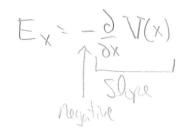19) The graph in the figure shows the variation of the electric potential V(x) (in arbitrary units) as a function of the position x (also in arbitrary units). Which of the choices below correctly describes the orientation of the x-component of the electric field along the x-axis?



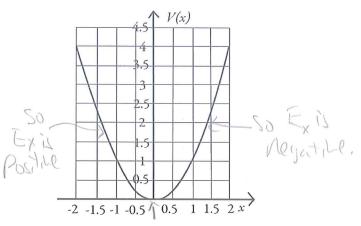

A)  $E_x$  is negative from x = -2 to x = 2.

- B)  $E_x$  is positive from x = -2 to x = 2.
- $\mathbb{C}$   $E_x$  is positive from x = -2 to x = 0, and negative from x = 0 to x = 2.
- D)  $E_x$  is negative from x = -2 to x = 0, and positive from x = 0 to x = 2.

20) A 9.0 V battery is connected to two resistors in series. If the resistors have resistances of 570.0  $\Omega$  and 730.0  $\Omega$ , what is the voltage drop across the 730.0  $\Omega$  resistor?