

$V = IR$  (Voltage = (Current \* Resistance)

When discussing Voltage it is important to discuss "change in voltage" or "delta V"

To measure the overall "change in Voltage" of a circuit we should attach the red wire from the voltmeter to the beginning of the circuit (right after the power supply) and the black wire to the end of the circuit (right before the other end of the power supply).