

(A)

From HW } Spherical Capacitor

Inner plate is sphere w/ $r_1 = 0.1 \text{ m}$

Outer plate is sphere w/ $r_2 = 0.115 \text{ m}$

\therefore "Separation" $d = 0.015 \text{ m}$

$$Q = 3.3 \text{ nC}$$

a.) Find $|\Delta V|$ between the two plates.

There are Two ways we can do this.

$V_{pt} = \frac{kQ}{r}$. This set the zero reference point @ $r = \infty$.


We cannot use this for point charges ($r=0$), BUT we don't have a point charge here! We CAN use this to find the voltage on the surface of each conducting sphere (an "equipotential" surface because the conductor is in electrostatic equilibrium). $E=0$ inside metal

$$V_{r_1} = \frac{kQ}{r_1} \quad V_{r_2} = \frac{kQ}{r_2}$$

$$\therefore |\Delta V| = \left| V_{r_2} - V_{r_1} \right| = \left| kQ \left(\frac{1}{r_2} - \frac{1}{r_1} \right) \right| = 38.7 \text{ volts}$$

(B)

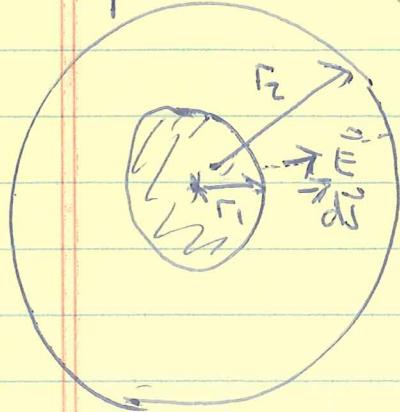The other way is to use Gauss to find \vec{E} between the spheres and then do a path integral.



$$|\vec{E}| = \frac{kQ}{r^2}$$

Can write ' r ' and dr $|r|$ ' 'x' and dx . THIS IS $1 - \frac{a}{r}$

$$|DV_{r_1 r_2}| = \left| - \int_{r_1}^{r_2} \vec{E} \cdot d\vec{s} \right| = |\vec{E}||d\vec{s}| \cos(0)$$

$$\frac{kQ}{r^2} \hat{r} \cdot dx \hat{i}$$

SAME
RESULT

$$|DV_{r_1 r_2}| = \left| - \int_{r_1}^{r_2} \frac{kQ}{x^2} dx \right|$$

$$= \left| -kQ \left(-\frac{1}{x} \right) \Big|_{r_1}^{r_2} \right|$$

$$= \left| kQ \left(\frac{1}{r_2} - \frac{1}{r_1} \right) \right| = \underline{\underline{38.7 \text{ volts}}}$$

(J)

b) Energy stored in capacitor is $\frac{1}{2} C \Delta V^2$.
There ARE equivalent expressions BUT

Will you (or I) ever remember them??

(C)

If we learn to work from concepts and equations we remember we will be able to do this stuff until the day we die (D). No worries about being lost in a class two semesters from now!

$$C = \frac{Q}{DV} = \frac{3.3 \times 10^{-9}}{38.7} = 8.527 \times 10^{-11} \text{ farads}$$

(F)

$$\therefore \text{Energy} = \frac{1}{2} CV^2 = \frac{1}{2} \times 8.527 \times 10^{-11} \times 38.7^2 = 6.39 \times 10^{-8} \text{ joules}$$

You could look back @ this calculation and write a general expression for

The capacitance of a spherical capacitor.

$$C = \frac{Q}{DV} = \frac{Q}{kQ(\frac{1}{r_1} - \frac{1}{r_2})} = \frac{4\pi\epsilon_0}{(\frac{1}{r_1} - \frac{1}{r_2})}$$

I am writing as a positive #

If there were no second plate, would this charged sphere still have a capacitance?

YES! Let $r_2 \rightarrow \infty$ and we have


$$C_{\text{sphere}} = 4\pi\epsilon_0 r_1$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

1a)

Given an arrangement of capacitors, find the charge and voltage on each.


Continued
from Monday

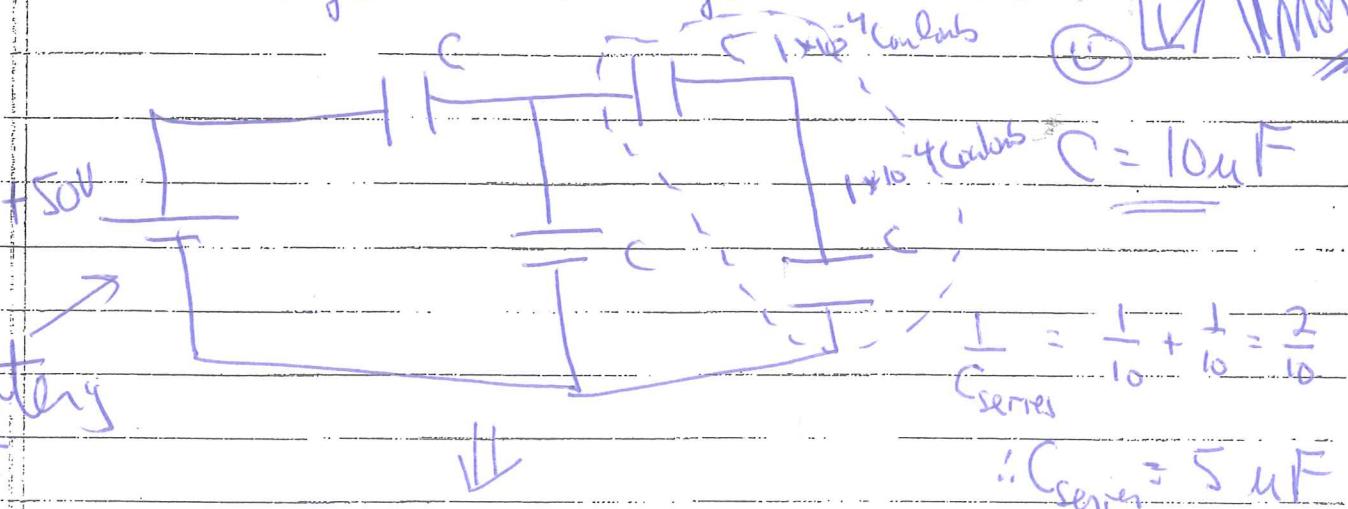

for $10 \mu\text{F}$

$$Q = CV \\ = 10 \times 10 \times 2 \\ = 2 \times 10^{-4} \text{ C}$$
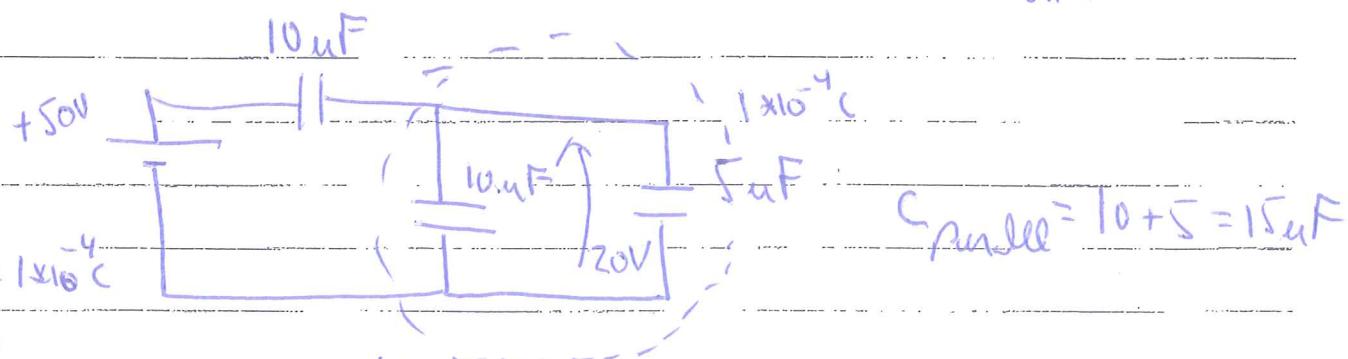
$$\text{For } 5 \mu\text{F} \quad Q = 1 \times 10^{-4} \text{ C}$$





for $10 \mu\text{F}$

$$Q = CV \\ \text{if } V_{10 \mu\text{F}} = \frac{3 \times 10^{-4} \text{ C}}{10 \times 10^{-6} \text{ F}} \\ = 30 \text{ Volts}$$

For $15 \mu\text{F}$
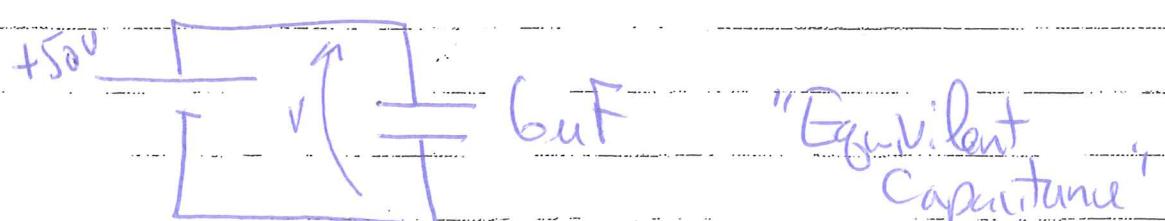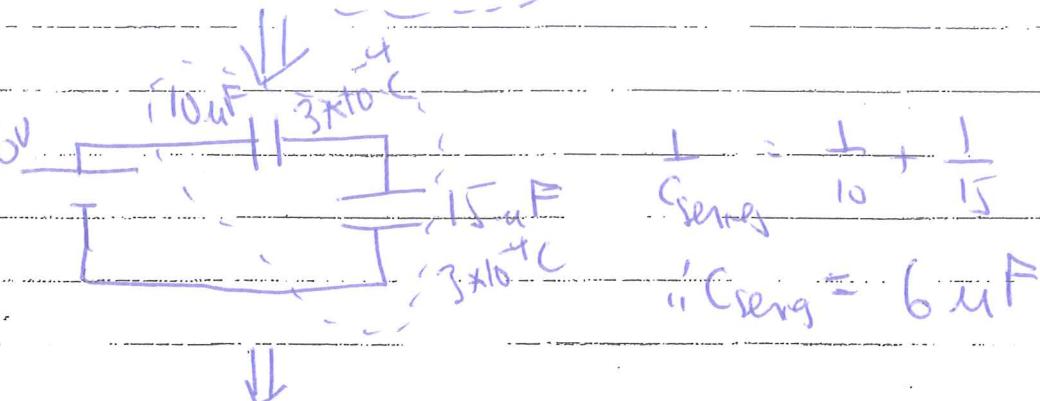
$$\text{so } V_{15 \mu\text{F}} = 20 \text{ Volts}$$




$$V = 50 \text{ Volts}$$

$$Q = C \times V = 3 \times 10^{-4} \text{ coulombs}$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%). (11)

Rules \Rightarrow Why?

"Series have the same charge"

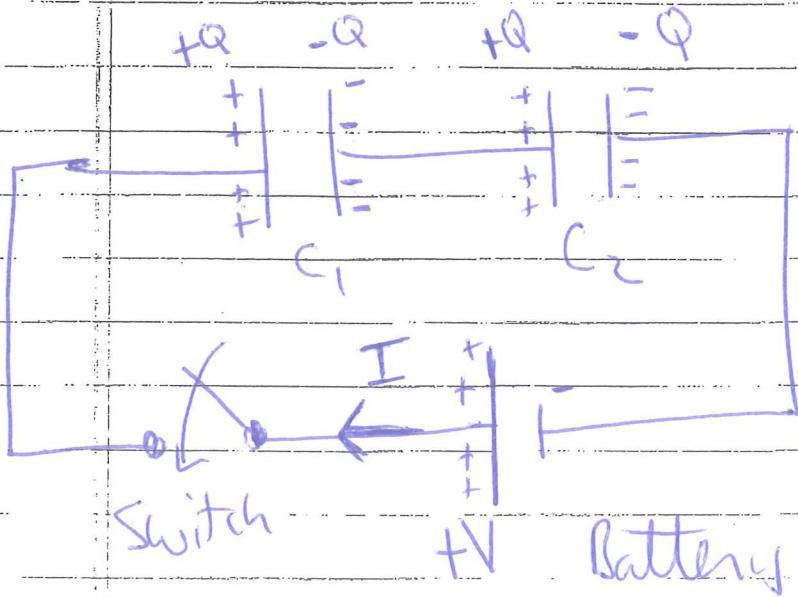

Current = $\frac{\text{Amount of charge passing by}}{\text{time}}$ || coulombs
(I) || "second"
SI. || "ampere"
(A)

ALWAYS assume that positive charges


are moving, "Conventional Current"

* Eventually, capacitors will fully charge and no current will flow in this circuit.


Resistance: A number indicating the difficulty with which charges move through objects (wires, ...)

Resistivity
Material Property
 $\equiv \frac{R}{lS}$

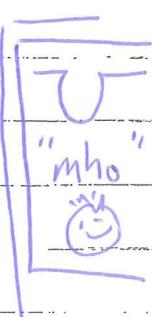Large Resistance \Rightarrow Very difficult *
DEPENDS on Geometry, composition, and
on temperature. SI \Rightarrow "ohm"
 Ω



A model for conduction:

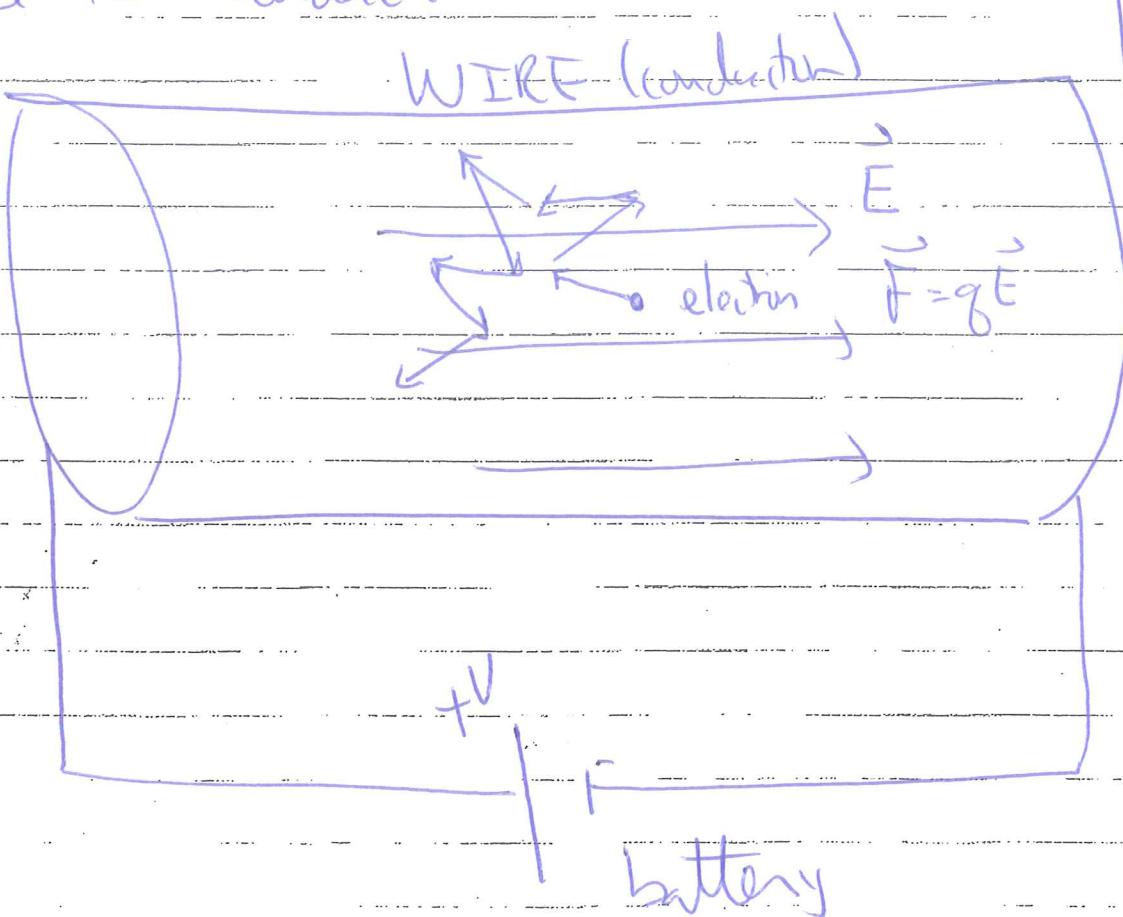

Collisions \Rightarrow "Ohmic heating"
* Mean free path
* Drift velocity

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%). (13)


DC \Rightarrow direct current \Rightarrow flows in one direction.

AC \Rightarrow alternating current

Resistor (light bulb, heater, toaster, ...)




Series

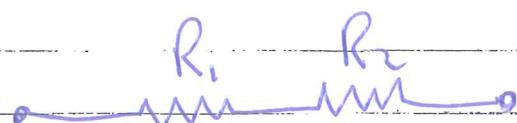


$$R_{\text{series}} = R_1 + R_2 + \dots$$

Parallel

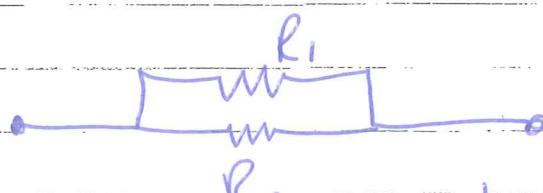


$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

EX:

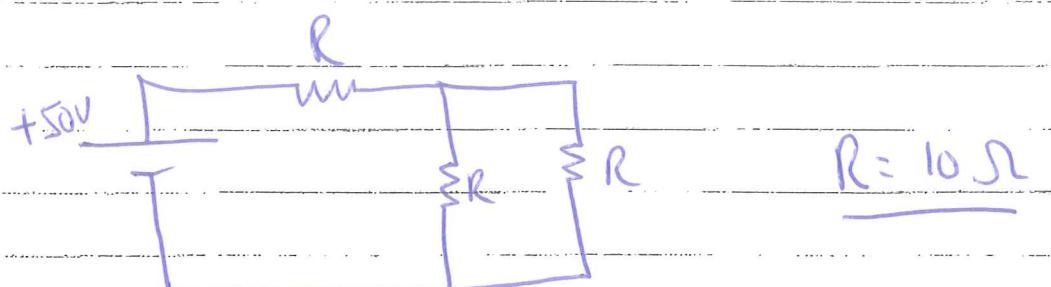

Find the current through and voltage across each resistor.

Ohm's Law: $\Delta V = IR$

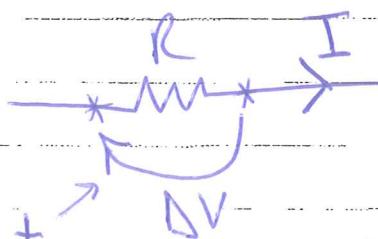

Solved like previous capacitor problem.

- Find equivalent resistance (pictures)
- Work 'backwards' using the rules

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%). 14

QJ

SEE PRACTICE


Rules: Resistors in series have same current. Resistors in parallel have same voltage.

+ Monday HW

Also ohm: Power =

Energy delivered
time

joules
sec
"watt"
(W)

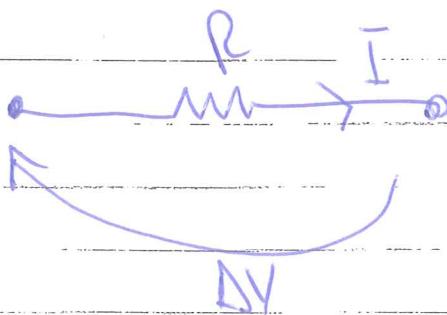

$$\text{Power} = \vec{I}^2 R = IAV = \frac{\Delta V^2}{R}$$


EX. Simple DC Circuit.



Find the current through the 5Ω resistor

$$\frac{1}{R_{II}} = \frac{1}{3} + \frac{1}{2}$$

$$\therefore R_{II} = 1.2\Omega$$

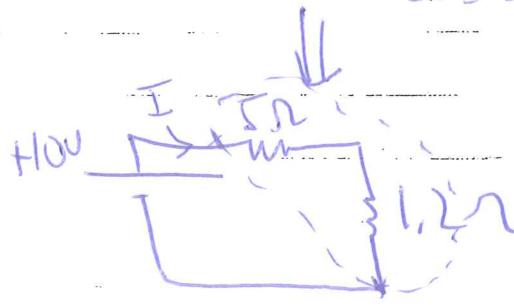

Solve QJ

$$10 = I(5 + 1.2)$$

$$I = 1.6 \text{ A}$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

15

Power to 5Ω ?

Power delivered to circuit by battery?

$$P_{5\Omega} = I^2 R = (1.6)^2 \underline{5} = \underline{\underline{12.8 \text{ watts}}}$$

$$P_{\text{battery}} = IV = (1.6)(10) = \underline{\underline{16 \text{ watts}}}$$

Counting
losses

$$P_{12\Omega} = ? \rightarrow \underline{\underline{3.2 \text{ watts}}}$$

Model for circuits

- Perfect wires ($R=0$). The wire is an equipotential surface (Voltage is constant along the wire). Thus the P.E. of a charge is constant along the wire. WIRES \Rightarrow Table tops
Charges \Rightarrow Marbles

- Get or give energy when crossing circuit element (ΔV)

Rules for Counting gain/loss :




 WALK $\Delta V = -IR$

$\Delta V = +IR$ WALK 

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

16

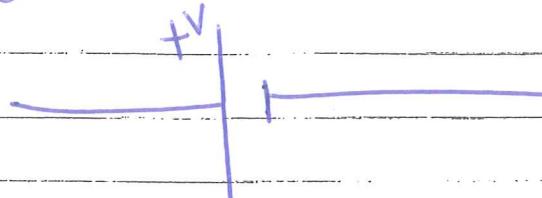A battery's job is to maintain a constant voltage across terminals REGARDLESS of current.




Walk $\Delta V = -V$

WALK $\Delta V = +V$

~~w1800~~ Kirchhoff's Loop rule (ch.26) ~~↙~~ ~~↖~~
(Voltage law)

$\sum V = 0$ Sum of the voltages around any closed loop in a circuit is ZERO.


Kirchhoff's junction rule

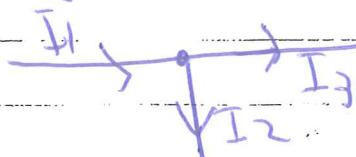

What goes in,
comes out.

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%). (17)

Find the current through each resistor.

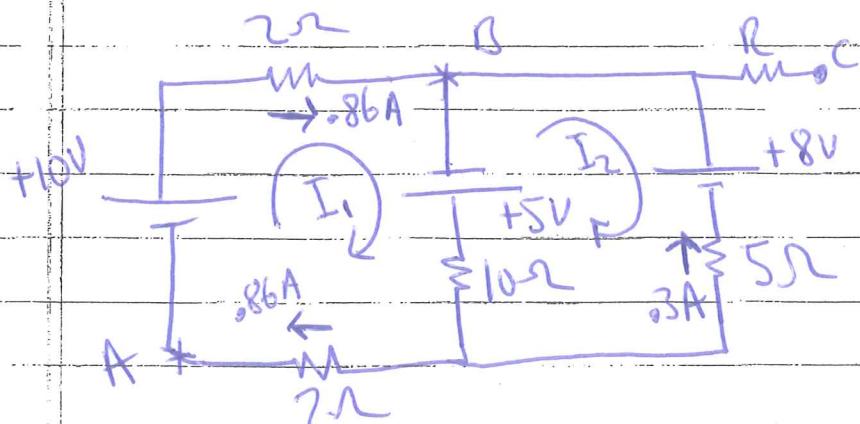

Model circuit
w/ "mesh currents"

Loop Rule

Loop 1

$$+10 - 2I_1 + \underbrace{5 - 10I_1 + 10I_2 - 2I_1}_{\Delta V_{10\Omega}} = 0$$

$$\boxed{1} \quad -4I_1 + 10I_2 = -15$$

Loop 2

$$-8 - 5I_2 - \underbrace{10I_2 + 10I_1 - 5}_{\Delta V_{10\Omega}} = 0$$

$$\boxed{2} \quad +10I_1 - 15I_2 = 13$$

$$\boxed{1} \Rightarrow I_2 = \frac{-15 + 14I_1}{10}$$


$$\text{use in } \boxed{2} \Rightarrow 10I_1 - 15 \left(\frac{-15 + 14I_1}{10} \right) = 13$$

$$-11I_1 + 22.5 = 13$$

$$I_1 = \underline{\underline{0.86 \text{ amps}}}$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%). (18)
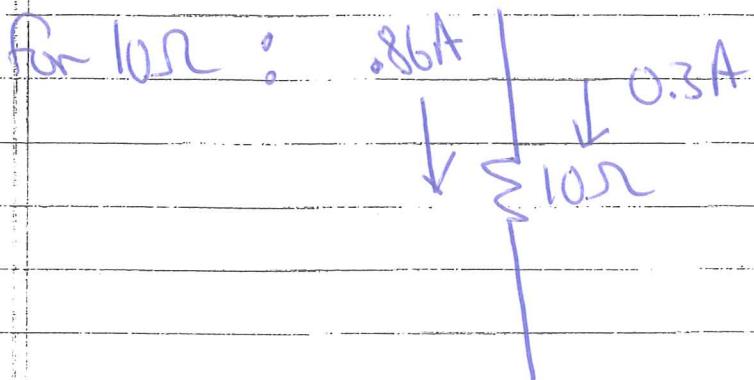
$$\therefore I_2 = \frac{-15 + 14I_1}{10} = -0.3 \text{ amps}$$



$$\text{Power}_{10\Omega} = ?$$

$$\Delta V_{A \rightarrow B} = ?$$

$$\Delta V_{B \rightarrow C} = ?$$

Electromotive Force (EMF)

Perfect Battery



Real batteries

