

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).



HW

25.64


$$R = 11 \times 10^3 \Omega$$

$$V = 16 \times 10^3 \text{ V}$$

$$r = 1600 \Omega$$

↑ "internal resistance"

SEE CANVAS ANNOUNCEMENT

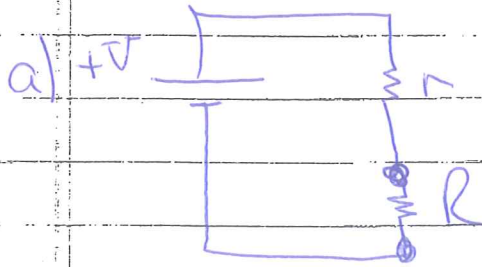

$$I = \frac{V}{(R+r)} = 1.27 \text{ A}$$

b.) $P = I^2 R = 17.74 \times 10^3 \text{ watts}$
To Person

c.) $r = ?$ but $I = 1 \times 10^{-3} \text{ A}$

$$V = I(R+r)$$


$$\frac{V}{I} = R + r$$

$$\therefore r = \frac{V}{I} - R = \frac{16 \times 10^3}{1 \times 10^{-3}} - 11 \times 10^3 = 1.6 \times 10^6 \Omega$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

(B)

HW 26.28 | 0.8A

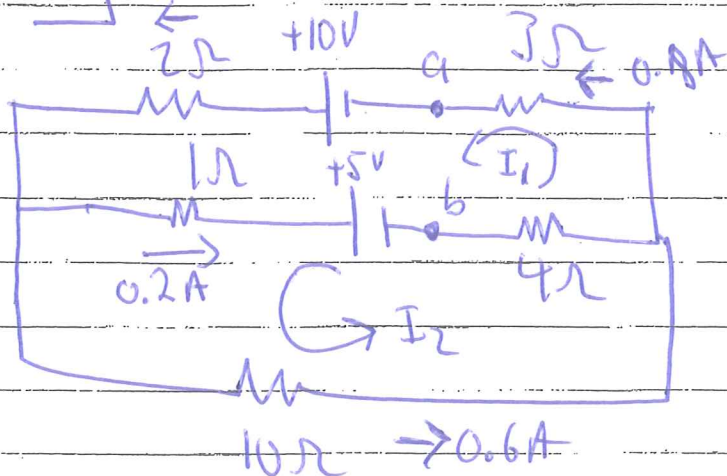

"mesh currents"

Loop #1

$$-3I_1 + 10 - 2I_1 - 1I_1 + 1I_2 - 5 - 4I_1 + 4I_2 = 0$$

V₁₀

$$\boxed{1} \quad -10I_1 + 5I_2 = -5$$

Loop #2

$$-10I_2 - 4I_2 + 4I_1 + 5 - 1I_2 + 1I_1 = 0$$

$$\boxed{2} \quad +5I_1 - 15I_2 = -5$$

Consider: $2 \times \boxed{2} + \boxed{1}$

$$+10I_1 - 30I_2 - 10I_1 + 5I_2 = -10 - 5$$

$$-25I_2 = -15$$

$$I_2 = 0.6A \quad (14)$$

$$\boxed{2} \Rightarrow I_1 = \frac{-5 + 15I_2}{5} = 0.8A \quad (15)$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

C

$$\Delta V_{a \rightarrow b} = + (0.8)(3) + (0.2)(4) = \underline{\underline{+3.2 \text{ volts}}}$$

$$\Delta V_{b \rightarrow a} = - (0.2)(4) - (0.8)(3) = \underline{\underline{-3.2 \text{ volts}}}$$


ΔV_{ab}

ΔV_{ba}



These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

Find The current Through each resistor.

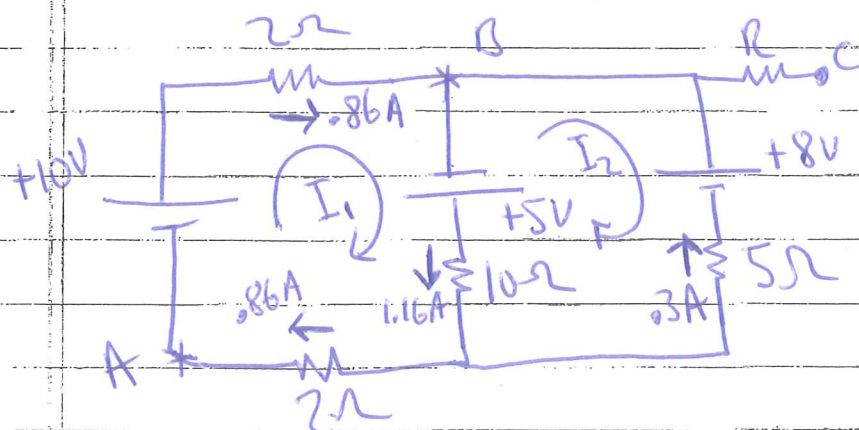

Model circuit
w/ "mesh currents"

Loop Rule

Loop 1

$$+10 - 2I_1 + 5 - 10I_1 + 10I_2 - 2I_1 = 0$$

$\Delta V_{10\Omega}$

$$\boxed{1} \quad -14I_1 + 10I_2 = -15$$

Loop 2

$$-8 - 5I_2 - 10I_2 + 10I_1 - 5 = 0$$

$\Delta V_{10\Omega}$

$$\boxed{2} \quad +10I_1 - 15I_2 = 13$$

$$\boxed{1} \Rightarrow I_2 = \frac{-15 + 14I_1}{10}$$

$$\text{use in } \boxed{2} \Rightarrow 10I_1 - 15\left(\frac{-15 + 14I_1}{10}\right) = 13$$

$$-11I_1 + 22.5 = 13$$


$$I_1 = \underline{\underline{0.86 \text{ amps}}}$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

18

2
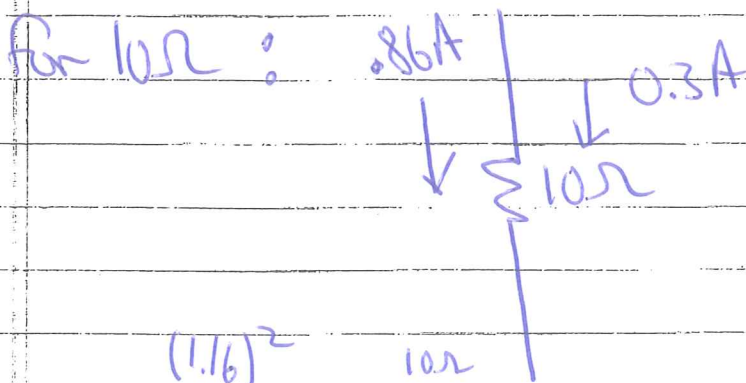
$$\therefore I_2 = \frac{-15 + 14I_1}{10} = -0.3 \text{ amps}$$



$$\therefore I_{10\Omega} = 1.16 \text{ A down}$$

Power $_{10\Omega} = I^2 R = 13.5 \text{ W}$


Electromotive Force (EMF)

$$\Delta V_{A \rightarrow B} = +10 - 0.86(2) = 8.28 \text{ V}$$

↳ Perfect Battery

$$\Delta V_{B \rightarrow C} = -(0)R = 0 \text{ V}$$

Real batteries

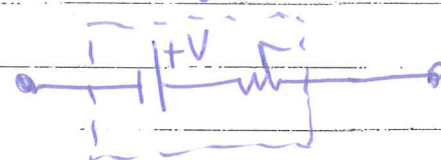

$$\vec{V} = V_x \hat{i} + V_y \hat{j} + V_z \hat{k}$$

$$\vec{B} = B_x \hat{i} + B_y \hat{j} + B_z \hat{k}$$

$$\vec{V} \times \vec{B} = \begin{vmatrix} +\hat{i} & -\hat{j} & +\hat{k} \\ V_x & V_y & V_z \\ B_x & B_y & B_z \end{vmatrix} = +\hat{i} \begin{vmatrix} V_y & V_z \\ B_y & B_z \end{vmatrix} - \hat{j} \begin{vmatrix} V_x & V_z \\ B_x & B_z \end{vmatrix} + \hat{k} \begin{vmatrix} V_x & V_y \\ B_x & B_y \end{vmatrix}$$

$$\vec{V} \times \vec{B} = +\hat{i} (V_y B_z - B_y V_z)$$

$$- \hat{j} (V_x B_z - B_x V_z)$$

$$+ \hat{k} (V_x B_y - B_x V_y)$$




is \perp to BOTH \vec{V} and \vec{B}

$$\vec{F} = q \vec{v} \times \vec{B} \quad \text{w/ expansion by minors}$$

OR

$$|\vec{F}| = q |\vec{v}| |\vec{B}| \sin \theta$$

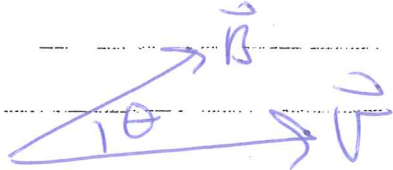


w/ direction assigned by a "right hand rule."

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

5

Convention



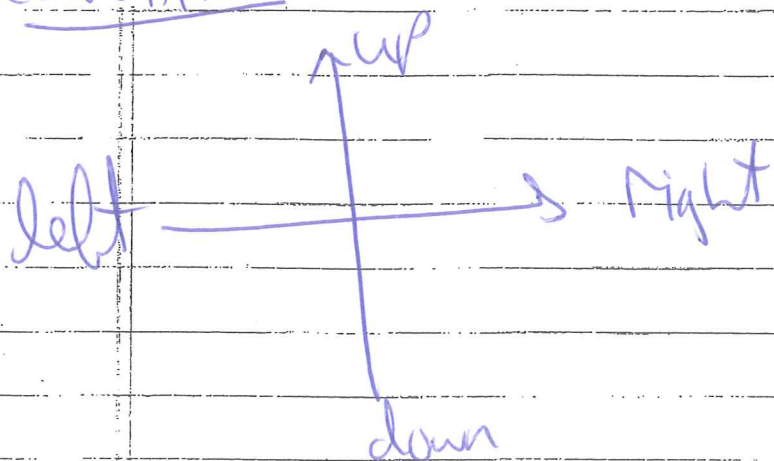


X IN (X)
• out (O)


IN to page
out of the page

Given: $\vec{C} = \vec{A} \times \vec{B}$


"Rt. hand rule"

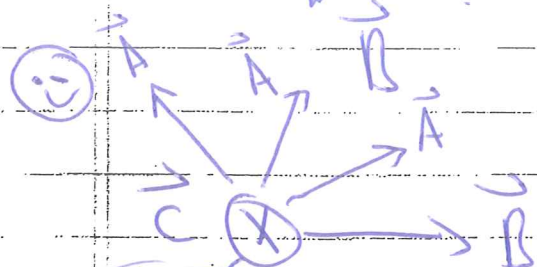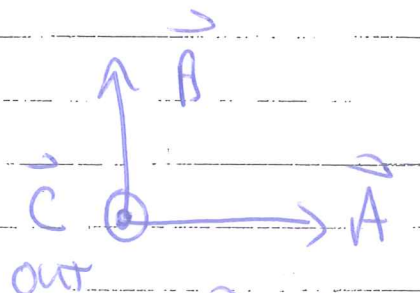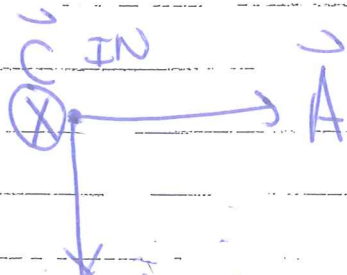

NO!!

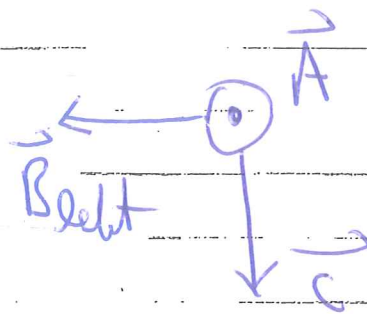
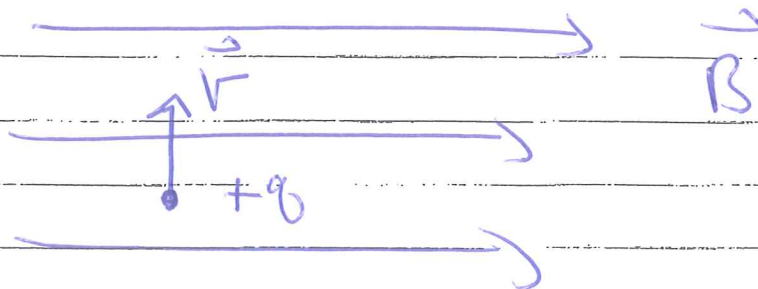
$$\vec{F} = q \vec{v} \times \vec{B} \quad \star$$




(i) \vec{B} right
 \vec{v} up
 \vec{F} IN
 Positive Charge

What if q was negative?

$$\vec{F} = (-q) \vec{v} \times \vec{B}$$

\vec{B} right
 \vec{v} up
 \vec{F} OUT!!

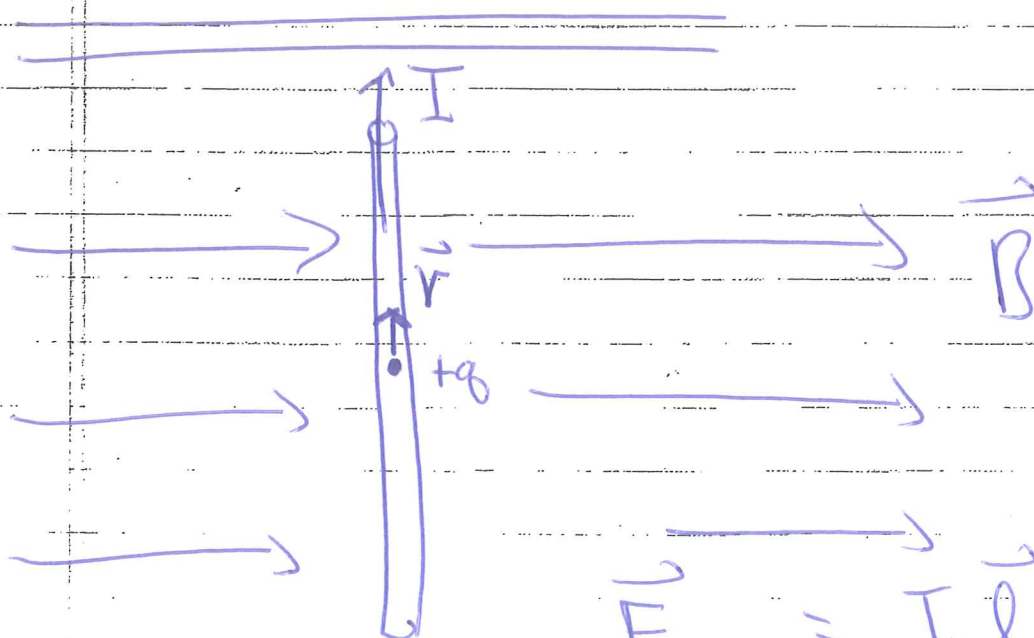


HW \star
 "Super position"

$$\vec{F}_{\text{wire}} = I \vec{\ell} \times \vec{B} \quad \star$$

[IN] $\vec{\ell}$ is length of wire
 IN direction of current

Paris ~ 1800

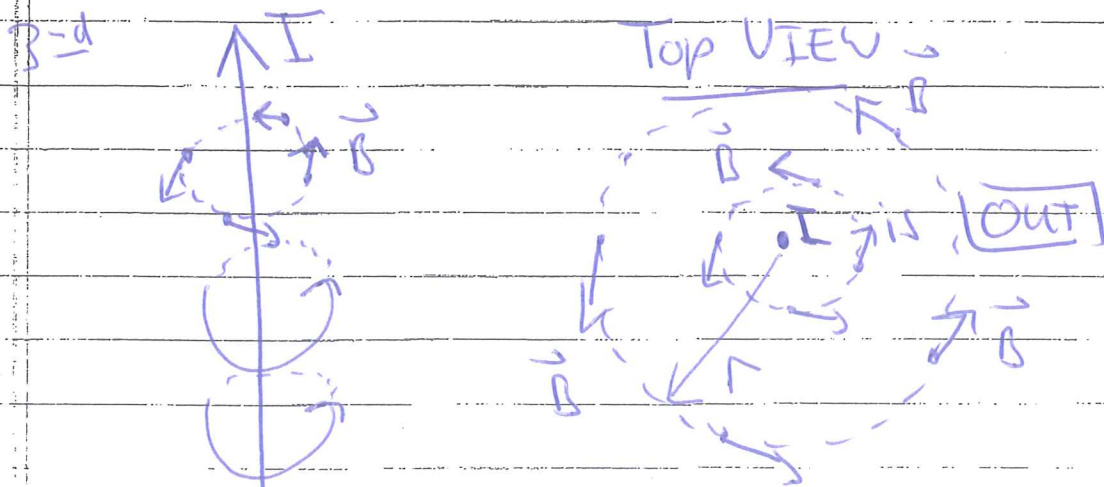
\vec{B} produced by wire carrying a current I :



= Empirical (it worked)

$$|\vec{B}|_{\text{wire}} = \frac{\mu_0 I}{2\pi r}$$

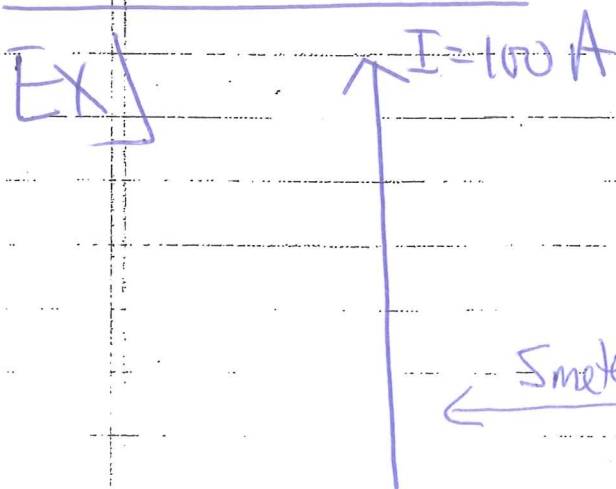μ_0 = permeability of free space
($4\pi \times 10^{-7}$)




At this instant in time, what is the magnetic force on the charge?

$$\vec{F} = q \vec{v} \times \vec{B}$$

a) location of q , $\vec{B} = \frac{\mu_0 I}{2\pi r} = \frac{4\pi \times 10^{-7} (100)}{2\pi (5)} \text{ [IN]}$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

78

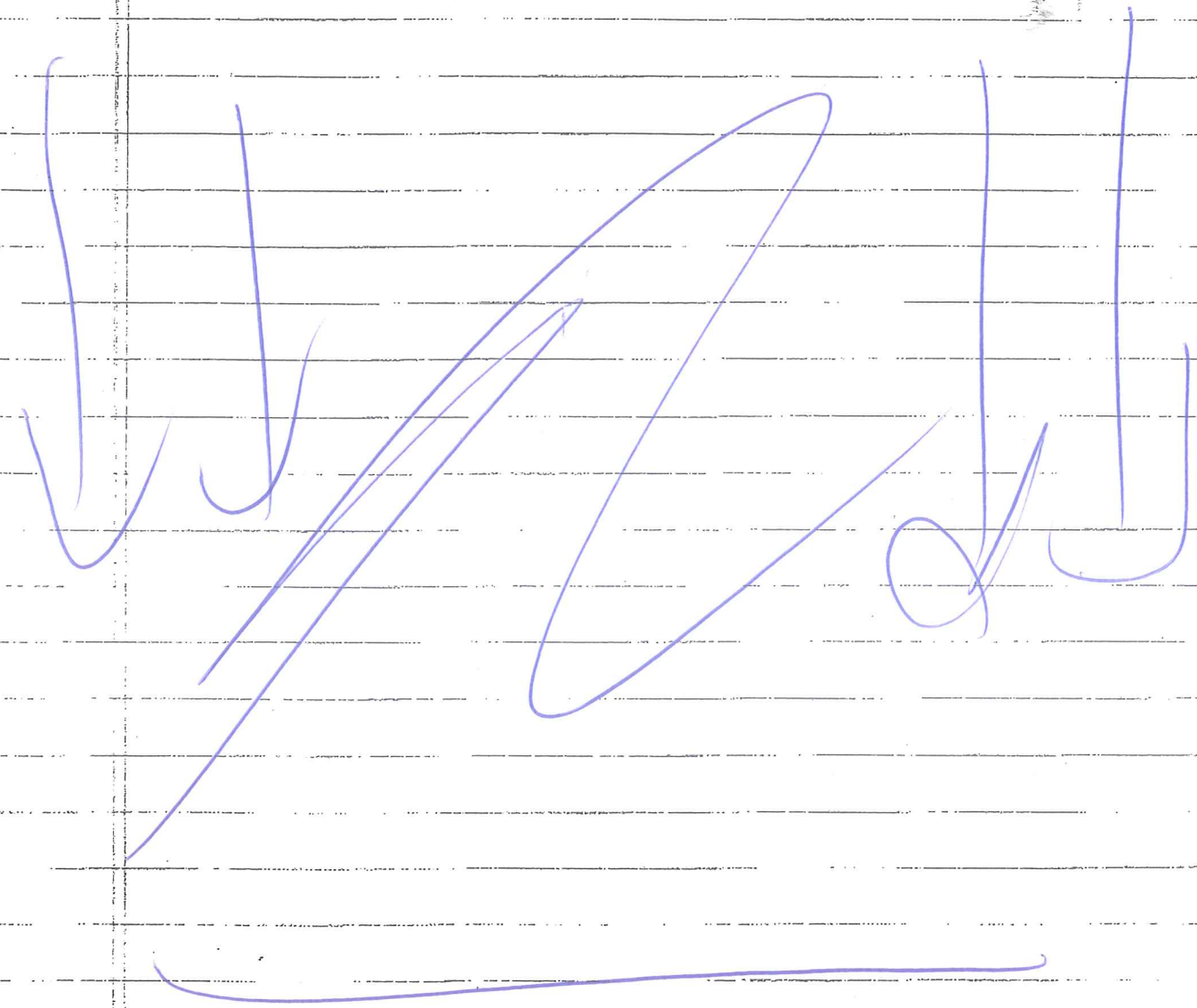

$$\vec{B} = 4 \times 10^{-6} \text{ tesla } \boxed{\text{In}} @ q$$


$$\therefore \vec{F} = (10)(25 \boxed{\text{right}}) \times (4 \times 10^{-6} \boxed{\text{In}}) \uparrow ? \text{ You OK?}$$

$$[q|\vec{v}||\vec{B}|\sin\theta] \Rightarrow 10(25)(4 \times 10^{-6})\sin(90) \boxed{\text{up}} \\ = 1 \times 10^{-3} \text{ Newtons } \boxed{\text{up}} \text{ Answer}$$

These are NOT notes. They are a visual aid(20%) for a verbal explanation(80%).

8

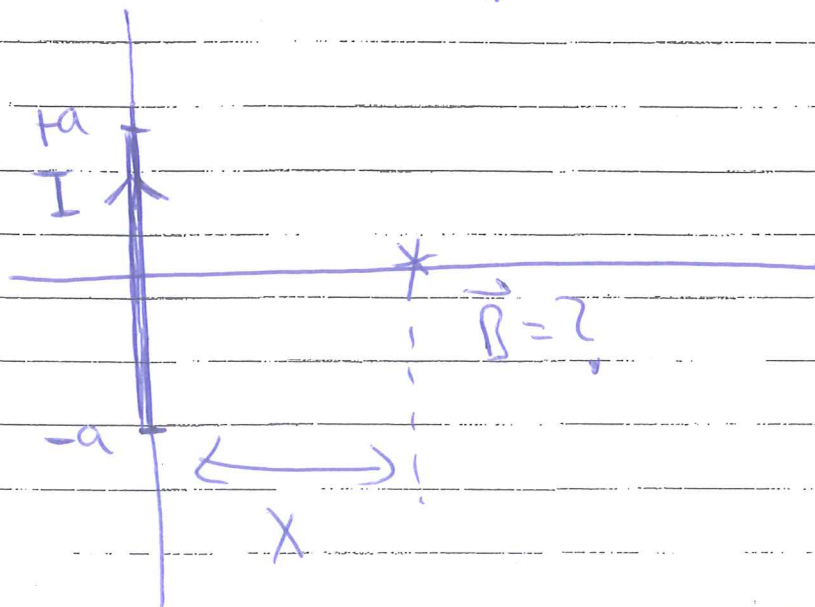EX] A wire of length $2a$ carries a current I . What is \vec{B} a distance x from its mid point?



~~not~~ "short wire"

Biot-Savart Law

$$d\vec{B} = \frac{\mu_0 I}{4\pi r^2} d\vec{\ell} \times \hat{r}$$

a small step in direction of I