

**Question 5****1 pts**

How will the multimeter be wired into the circuit to measure voltage across a resistor, in parallel or in series?

☒ Parallel

☐ Series