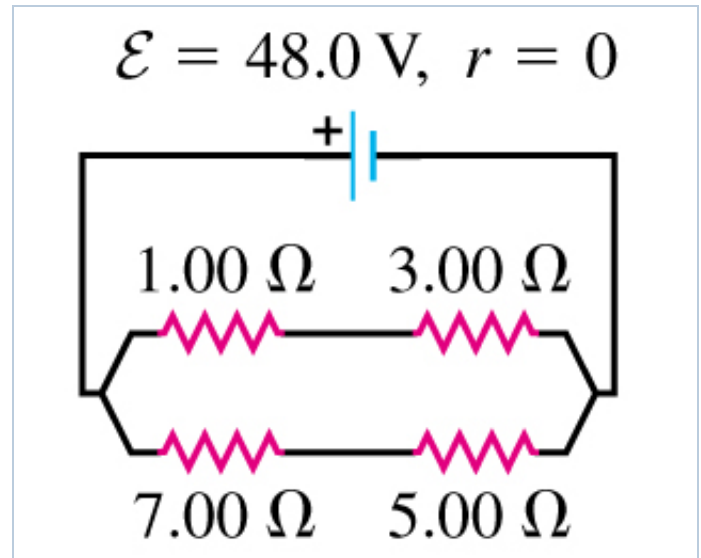


## Exercise 26.14

### Part A

Compute the equivalent resistance of the network in the figure. The battery has negligible internal resistance.



ANSWER:

$$R_{\text{eq}} = 3.00 \ \Omega$$

**Correct**

### Part B

Find the current in 1.00  $\Omega$  resistor.

ANSWER:

$$I = 12.0 \text{ A}$$

**Correct**

### Part C

Find the current in 3.00  $\Omega$  resistor.

ANSWER:

$$I = 12.0 \text{ A}$$

**Correct**

---

**Part D**

Find the current in  $5.00\Omega$  resistor.

ANSWER:

$$I = 4.00 \text{ A}$$

**Correct**

---

**Part E**

Find the current in  $7.00\Omega$  resistor.

ANSWER:

$$I = 4.00 \text{ A}$$

**Correct**