

**Question 4****2 pts**

Given the circuit below, calculate the total current flowing through the circuit. Where $R_1 = 3.0\text{ k}\Omega$ and $V = 3.0$ Volts. Give your answer in miliamps, and round your answer to the second decimal place.